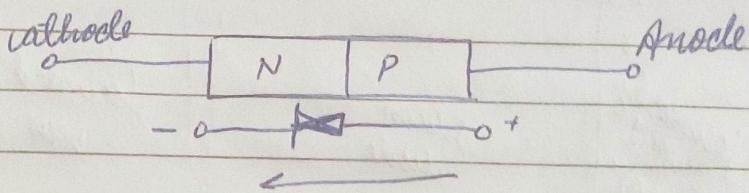


Unit :- 1Q. PN Junction diode :-

In a piece of semiconductor, if one half is doped with  $P$ -type impurity and other half is doped with  $N$ -type impurity, a  $PN$  junction is formed. The plane dividing the two half or zones is called  $PN$  junction.




- In  $P$  side, majority carrier is hole and minority carrier is electron ( $e^-$ )
- In  $N$  side, majority carrier is electron and minority is hole.
- Net Electron move from  $N$  to  $P$ . from high conc. to low.
- Silicon and germanium are two semiconductor material

Forward biased junction diode :-


When a diode is connected in a forward bias condition a negative voltage is applied to the  $N$ -type region material and a positive voltage is applied to the  $P$ -type material. If this external voltage becomes greater than the off value of the potential barrier, approx. 0.7 volts for silicon and 0.3 volts for germanium, the potential barrier opposite will be overcome and current will start to

to flow. This is because the negative voltage pushes or repels electrons towards the junction giving them the energy to cross over and combine with the holes being pushed in the opposite direction towards the junction by the positive voltage. This results in a electrostatic curve of zero current following up to this voltage point called the 'knee' on the static curve and then a current flow through the diode with little increase.

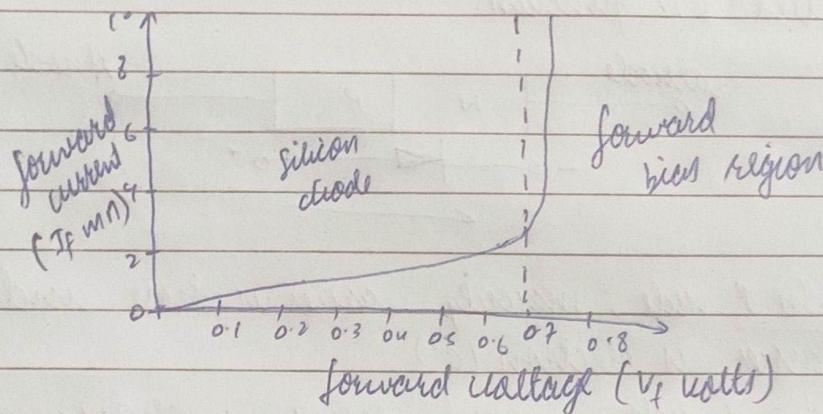

The application of a forward biasing voltage on the junction diode results in the depletion layer becoming very thin and narrow which represents a low impedance path through the junction thereby allowing high current to flow.

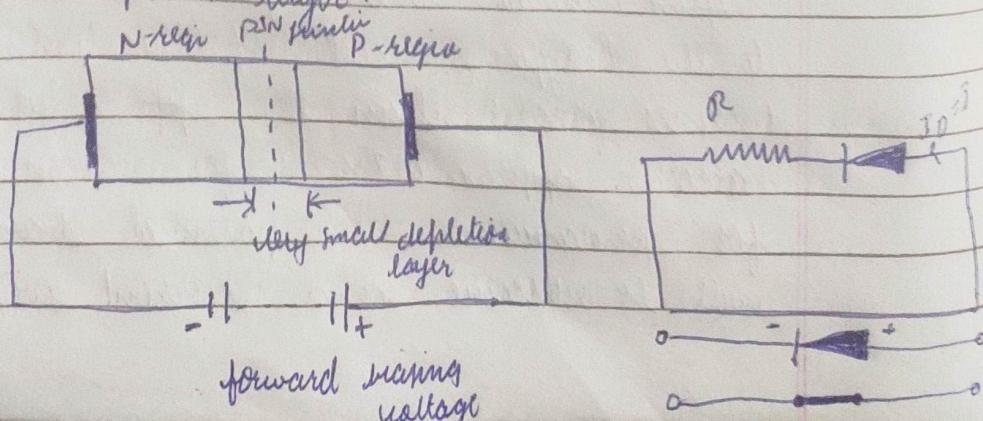
→ Forward biased junction diode showing a reduction in the depletion layer.




The condition represents the low resistance path through the PN junction allowing very large current flow through the diode with only a small increase in voltage. The actual potential difference across the
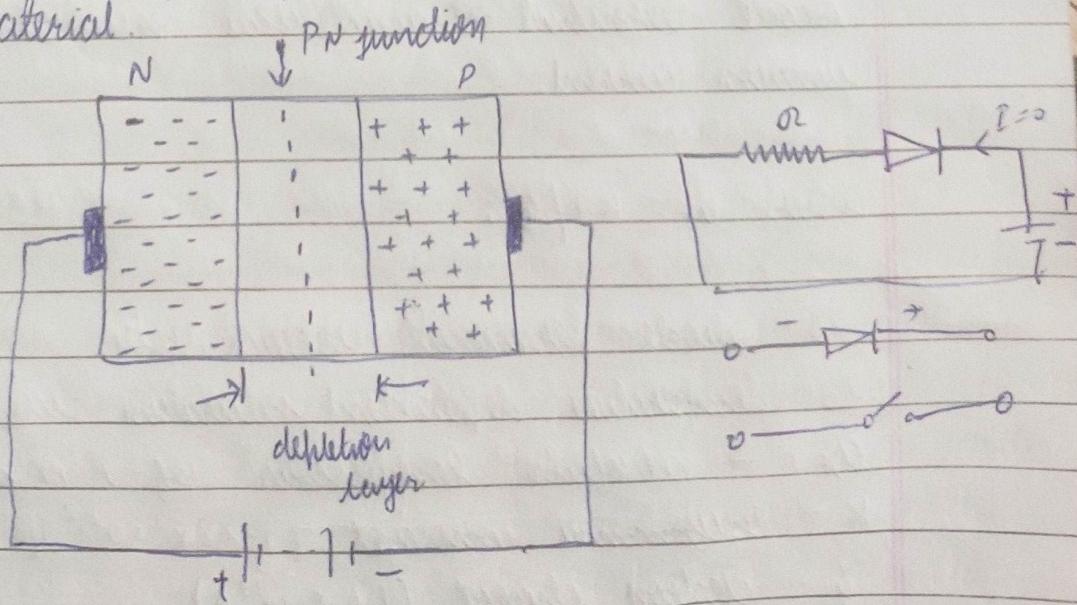
### PN Junction under Reverse Bias:

when a diode connected in reverse bias condition a positive voltage is applied to the N-type material and a negative voltage is applied to the P-type material. The positive voltage applied to the N-type material attracts electron toward the positive electrode and away from the PN junction while the holes in the P-type are also attract away from the junction towards the negative electrode. The net result is that the depletion layer grows wider due to a lack of electron and holes and present a high impedance path almost an insulator. This result is that a high potential barrier is created preventing current from flowing through the semiconductor material.



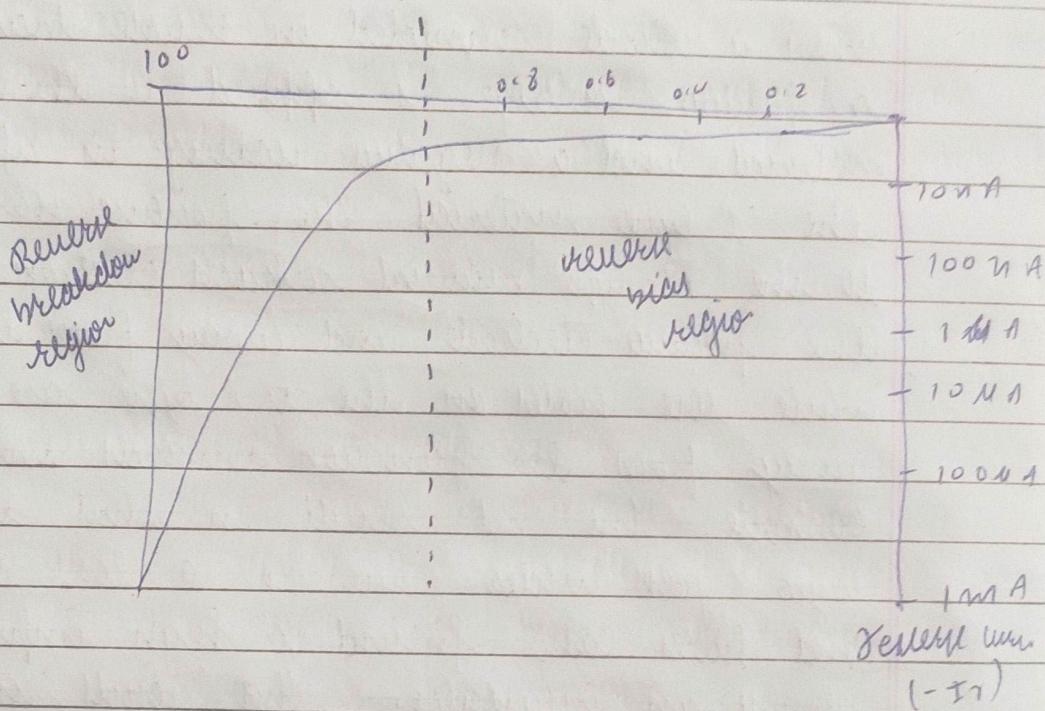The condition represents a high resistance value to the PN junction and permits practically zero current flow through the junction diode with an increase in junction diode bias voltage. However, a very small leakage current does flow through the junction which can be measured in microamperes (μA).



V-I characteristics :-

circle terminal characteristics equation for circle function current:

where  $v_f = kT/q$ ;


$V_D$  diode terminal voltage, mV.

## To temperature dependent saturation current, part

MAT - absolute temperature of P-N junction


$k = \text{Boltzmann's constant } (1.38 \times 10^{-23} \text{ J/K})$

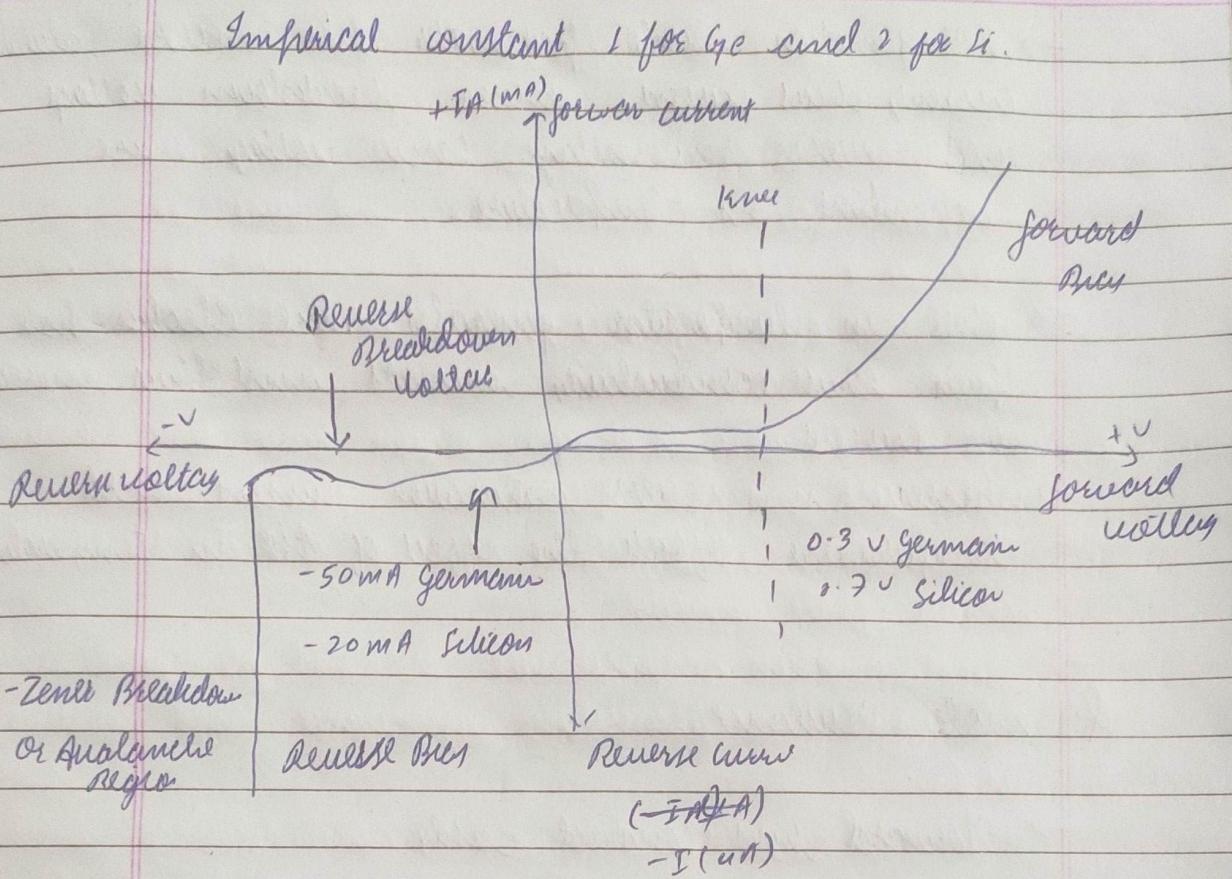$q$  - electron charge ( $1.6 \times 10^{-19} C$ )


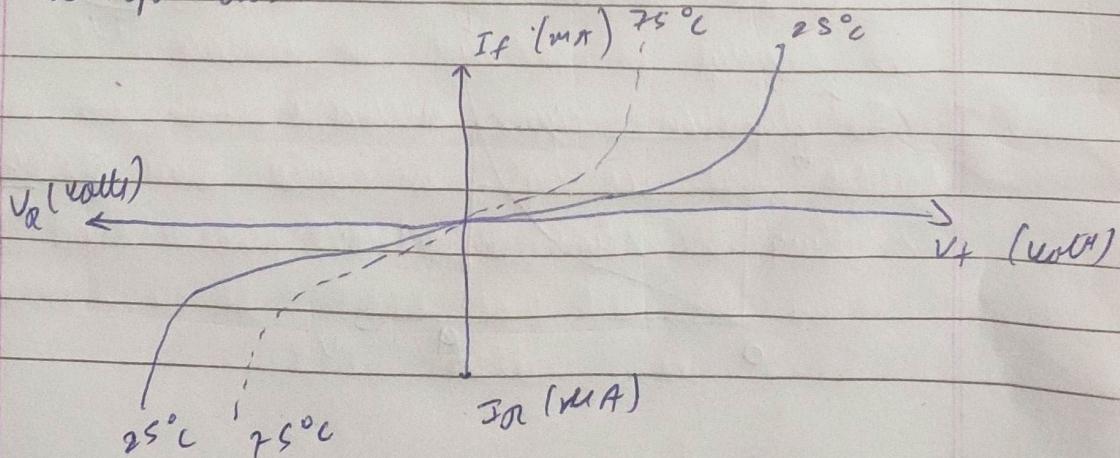
### Temperature Effect on a diode :-

Temperature can have a marked effect on the characteristics of a silicon semiconductor diode as. It has been found experimentally that the reverse saturation current  $I_0$  will just about double in magnitude every  $10^\circ\text{C}$  increase in temperature.



→ PN junction diode parameters like reverse saturation current, bias current, reverse breakdown voltage and reverse bias voltage barrier voltage are dependent on temperature.

- Rise in temperature generates more electron-hole pairs thus conductivity increases and thus increase in current.
- Increase in reverse saturation current with temperature offsets the effect of rise in temperature.

### Q. Diode Resistance:-

→ Forward bias conduct easily.

If we supply DC then its Static Resistance


If we supply AC then its Dynamic Resistance

### \* D or static resistance :-

It is simply the ratio of DC voltage across the diode to the direct current flowing through it

$$R = \frac{V}{I}$$


$$R_{dc} = \frac{V_{dc}}{I_{dc}}$$

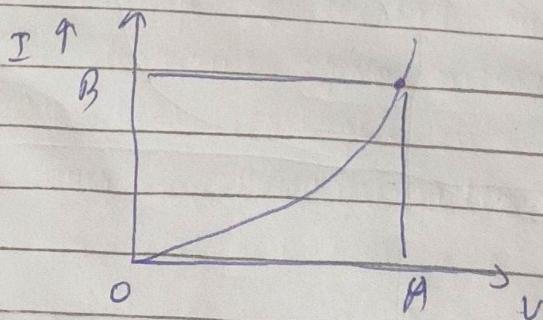

$$R = \frac{OA}{OB}$$
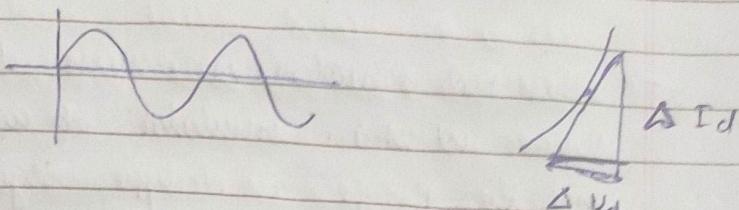
## \* AC or dynamic Resistance

Resistance offered by a diode to changing forward current.



$$R = \frac{1}{\text{slope}} = \frac{\Delta V}{\Delta I} = \frac{\text{change in voltage}}{\text{change in current}}$$

$$R = \frac{dV}{dI} = \frac{n V_T}{I_0 e^U / n V_T}$$

$$R_{dc} = \frac{V_{dc}}{I_{dc}}$$

→ Reverse bias resistance high / block the flow of current.

When we connect the diode in reverse bias condition, there will be a small current flowing through it which is called the reverse leakage current.

Due to this current flow, the diode exhibits reverse resistance characteristic.

$$R_r = \frac{V_r}{I_r}$$


where  $V_r$  and  $I_r$  are the reverse voltage and reverse current.

## Transition and diffusion capacitance :-
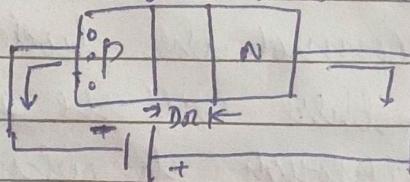
### Transition capacitance:

(or space charge)

- When P-N junction is reverse biased the depletion region act as an insulator or as a dielectric medium and the P-type or N-type region have low resistance and act as the plates.
- Thus this P-N junction can be considered as a parallel plate capacitor.
- This junction capacitance is called as space charge capacitance or transition capacitance and is denoted as  $C_T$ .
- Since reverse bias causes the majority charge carriers to move away from the junction, so the thickness of the depletion region denoted as  $w$  increases with the increase in reverse bias voltage.




- This incremental capacitance  $C_T$

$$C_T = \frac{dQ}{dV}$$

where  $dQ$  is the increase in charge and  $dV$  is the change or increase in voltage.

- The depletion region increases with the increase in reverse bias voltage. In reverse bias potential the resulting transition capacitance decreases.

## → Diffusion capacitance.

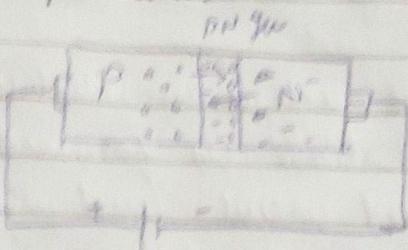

Density of charge carriers is higher at PN junction and reduces or decays at the distance increases

→ when the junction is forward biased, a capacitance comes into play, that is known as diffusion capacitor denoted as  $C_D$ . It is much greater than the transition capacitance

$C_D \gg C_T$ . Thus  $C_T$  can be neglected in forward bias

→ during forward biased the potential barrier is reduced. The charge carrier move away from the junction and recombine



→ Thus in this case charge is stored in the both side of the junction and varies with the applied potential so as per definition change in charge with respect to applied voltage result in capacitance which here is called as diffusion capacitance.

→ The formula for diffusion capacitance is  $C_D = \tau I_D / n V_T$ , where  $\tau$  is the mean life time of the charge carrier,  $I_D$  is the diode current and  $V_T$  is the applied forward voltage and  $n$  is generation recombination factor.

→ The diffusion capacitance is directly proportional to diode current.
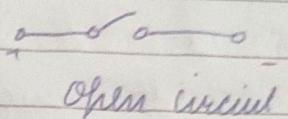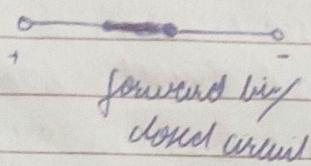
## Diode Switching times :-

- Diode can be act as an electrical switch.
- when the diode is forward bias it will act as a closed circuit and whenever it is in reverse bias it will act as an open circuit



- Forward biased diode indicate -on state  
Reverse biased diode indicate -off state.
- for conversion from on state to off state  
or off state to on we require two recovery time.

- ① Forward Recovery time ( $t_{fr}$ )
- ② Reverse Recovery time ( $t_{rr}$ )

### ① Forward recovery time ( $t_{fr}$ )

→ The time interval taken by the diode to switch from reverse biased (OFF) to a forward biased (ON) is called  $t_{fr}$ .

### ② Reverse recovery time ( $t_{rr}$ )

→ The time interval taken by the diod to switch from forward bias (ON) to a reverse biased (OFF) is called  $t_{rr}$ .


## Zener Diode :-

Zener diodes are normal PN junction diodes operating in a reverse biased condition.


Zener diode can also conduct when it is conducted in reverse bias above its threshold or breakdown voltage.

Semiconductor diode in reverse bias condition

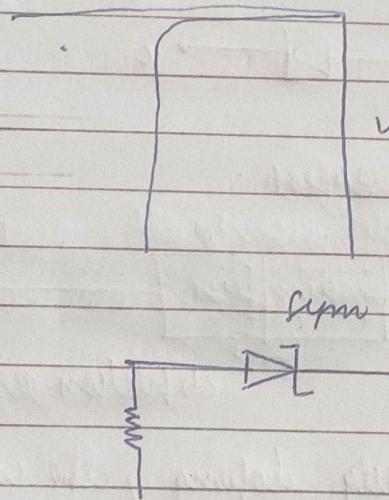- It is a ~~Special Purpose~~ diode, used for operation
- Doping done to have a sharp breakdown voltage



## Avalanche Breakdown

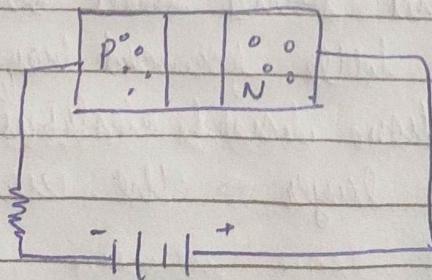

The majority charge carriers

Tunnel Diode:

[Esaki diode]


A Tunnel diode is a heavily doped P-N Junction diode

→ It has negative resistance characteristic.


due to tunneling effect.

→ Tunnel diode worked on based on the concept tunneling effect.

Symbol.

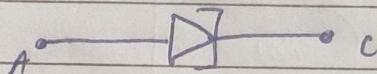

\* Tunneling Effect

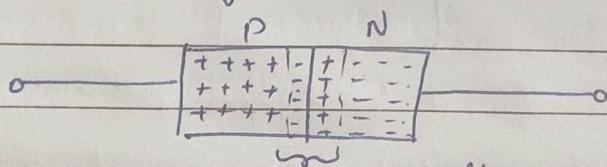


depletion Region.

→ Due to heavily doping, the width of the depletion region becomes very thin and an overlap occurs between the conduction band on the n-side and the valence band level on the p-side.


→ Under little forward bias condition, the conduction band electrons <sup>tunnel</sup> through the depletion layer → The current reaches minimum of  $I_P$ .

## Working Principle

\* Zero-bias

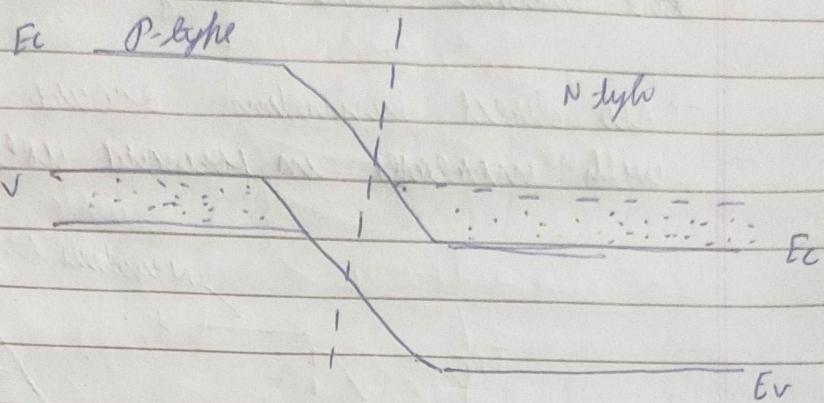

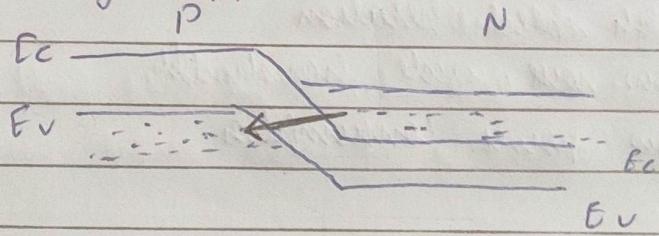- Due to overlapping, the conduction band electrons at n-side and valence band holes at p-side are at the same energy level.
- Therefore is no current flow.
- Small voltage applies




- Under small forward bias condition, the conduction band electrons tunnels through the depletion layer resulting the tunnel current.

\* High forward voltage :-

The current reaches maximum current at Peak voltage ( $V_p$ )
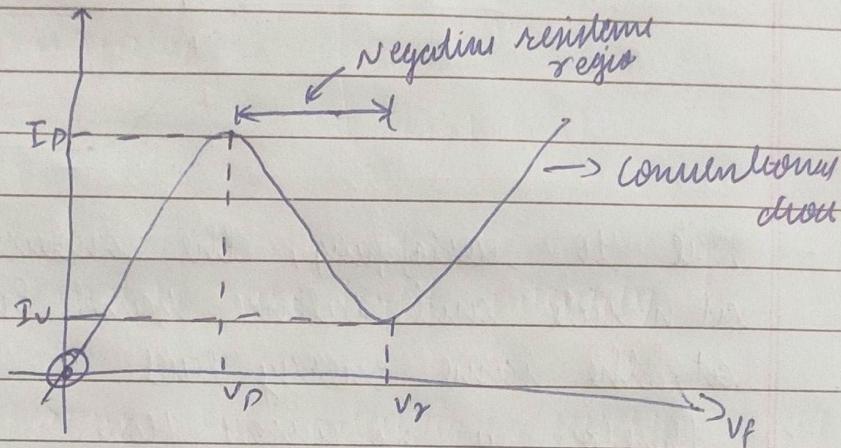
## V-I characteristics :-

- For further increase of forward bias the conduction band energy level are increased above the valence band energy level.
- No direct tunneling occurs so current decreases with increases in forward voltage till  $v_r$ .



### Advantages

- High speed operation
- low noise, wide bandwidth
- low power consumption

### Disadvantages :

- High cost
- The input and output are not isolated from each other


### Applications :-

- It can be used as tunnel diode reflection amplifiers (TDR's)
- used as logic memory storage device
- used as an ultra high speed switch

## # PHOTO DIODES:-


It is a device used to detect & convert light energy into electrical energy. It is operated under reverse bias below breakdown voltage.

Symbol:-

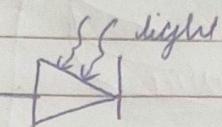

Construction :-

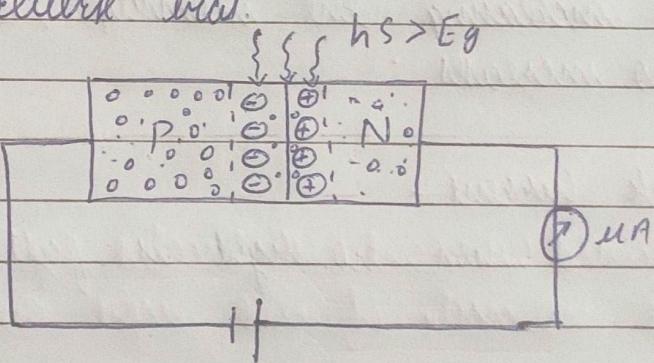A photodiode fabricated with a transparent cover to allow light to fall on the diode & operated under reverse bias.




Working :-

When a photodiode is illuminated with light with energy greater than the energy gap of the semiconductor then e-hole pair are generated due to the absorbtion of photons.

These charge carriers contribute to the reverse current.

## V-I characteristics:-

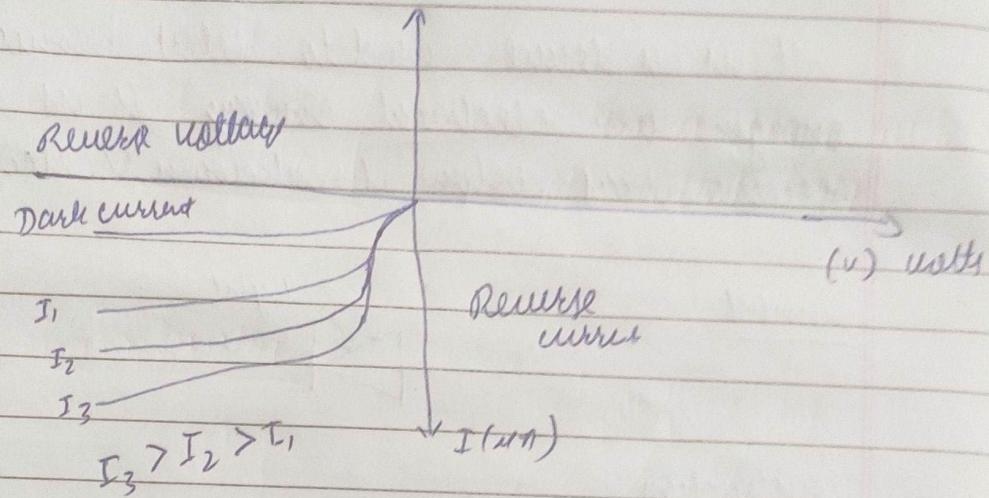

$I_1, I_2$  and  $I_3$  are light intensity

On increasing the intensity, reverse current also increases.

Dark current:-

When no light is fall on the junction.


Uses :-

- 1) In photodetection for optical signals
- 2) In demodulation for optical signals
- 3) In counting machines
- 4) In optical communication equipment

## # LED (light emitting diode)


It is heavily doped P-N junction diode which convert electrical energy into light energy. This diode emit light under forward biasing.

Symbol:-

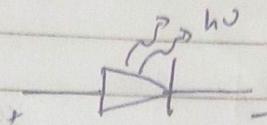

Construction:-

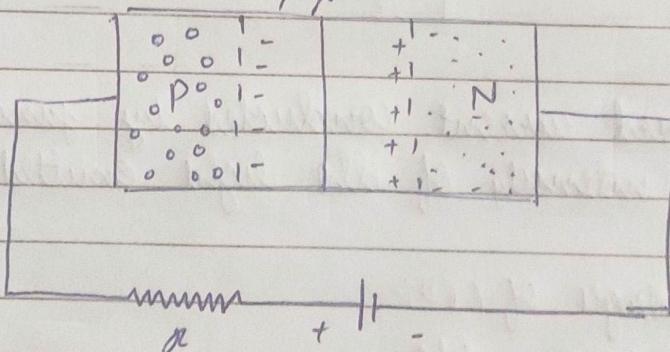In this P-N junction diode is connected from a battery through resistance R which control control the brightness of light emitted.



Working:-

When P-N junction is forward biased, electron & hole move towards opposite side of junction. There are excess majority carriers on the either side of junction boundary, recombine with majority carrier near the junction.

On recombination of e-h pair, the energy is given out in the form of light. The released energy is nearly equal to  $Eg$  energy gap.

$$E_g = h\nu$$


$$\therefore E_g = \frac{hc}{\lambda}$$

$$\boxed{\lambda = \frac{hc}{E_g}}$$

$$\nu_g = h\nu$$

This is the wavelength of emitted light.

V-T characteristics :-

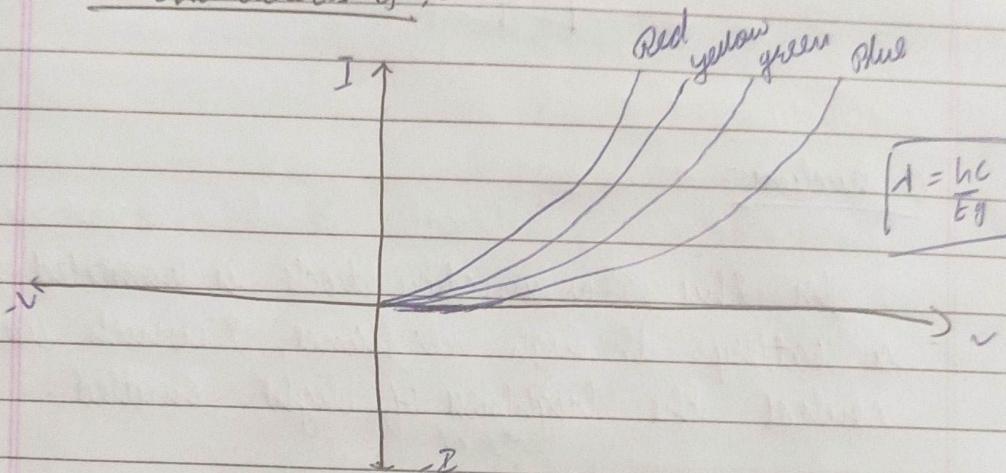

→ Forward current conducted by junction determined the intensity of the light emitted.

Advantages of LED:-

- 1 → long life
- 2 → operate on low operational voltage
- 3 → less power consumption
- 4 → cheap & easy to handle

Uses of LED:-


- 1 → In burglar alarm system
- 2 → calculator digital watches
- 3 → In traffic lights
- 4 → In remote control.

to full


## Classification of Rectifiers :-
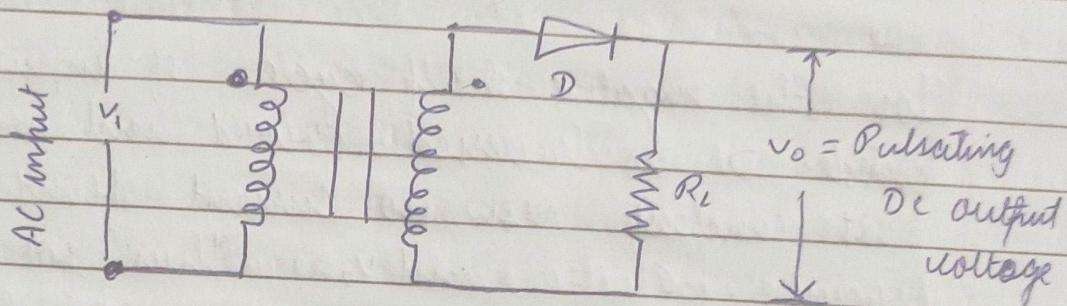
### P Half-wave Rectifier

A half wave rectifier is one, which converts a.c voltage into a pulsating voltage using only one half cycle of the applied a.c voltage.



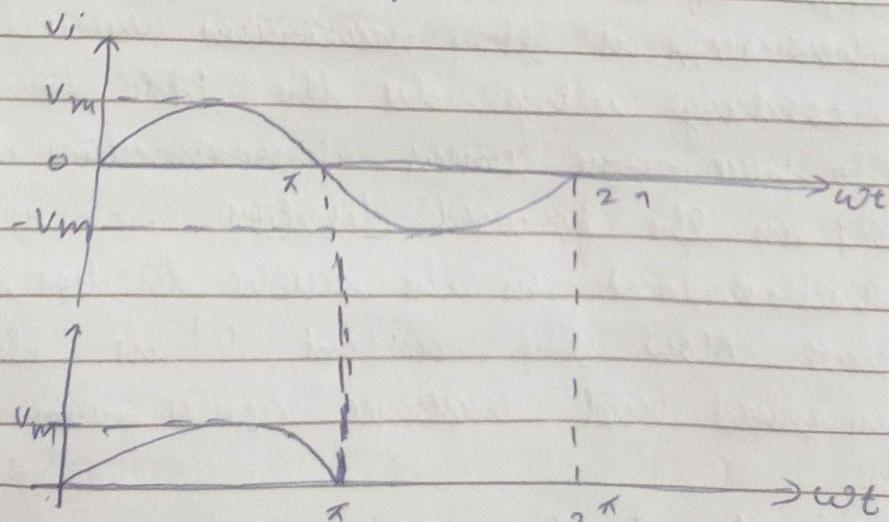The a.c voltage applied to the rectifier circuit using step down transformer - rectifying element i.e p-n junction diode and the source of a.c voltage , all connected in series . The a.c voltage is applied to the rectifier circuit using step - down transformer.



Input and output waveform of a Half wave rectifier.

## operation:-

For the positive half-cycle of input a.c. voltage, the diode D is forward biased and hence it conducts. Now a current flows in the circuit and there is a voltage drop across the waveform of the diode current (as) is shown in graph.


For the negative half cycle of input, the diode D is reverse biased and hence it does not conduct. Now no current flows in the circuit. i.e.  $i=0$  and  $v_o=0$ . Thus for the negative half-cycle no power is delivered to the load.

⇒ Full wave



A full-wave rectifier using the applied half cycles of this circuit with the help of a step transformer sinusoidalency but on in the second full wave
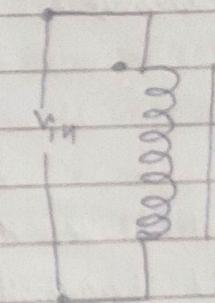
## Analysis

Let a sinusoidal voltage  $v = v_i$  be applied to the input of the rectifier. Then  $v = V_m \sin(\omega t)$  where  $V_m$  is the maximum value of the secondary voltage. Let the diode be ideal. Do piece-wise linear approximation with  $R_f$  in the forward direction, i.e. in the ON state and  $R_f \approx \infty$  in the reverse direction, i.e. in the OFF state. Now the current 'i' in the diode in the load resistance  $R_L$  is given by  $v = iR_L$



center tapped  
transformer

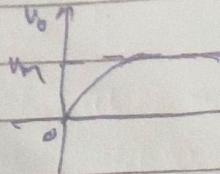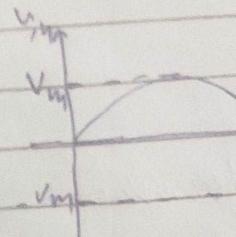

## Disadvantages

1. The ripple factor is high.
2. The efficiency is low.
3. The transformer utilization factor is low.

input a

## 2) Full wave rectifier

A full-wave rectifier converts an ac voltage into a pulsating dc voltage using both half cycles of the applied ac voltage. In order to rectify both the half cycles of ac input, two diodes are used in this circuit. The diode feeds a common load  $R_L$  with the help of a center-tap transformer. A center-tap transformer is the one, which produces two sinusoidal waveforms of same magnitude and frequency but out of phase with respect to the ground in the secondary winding of the transformer. The full wave rectifier is shown in the fig. below


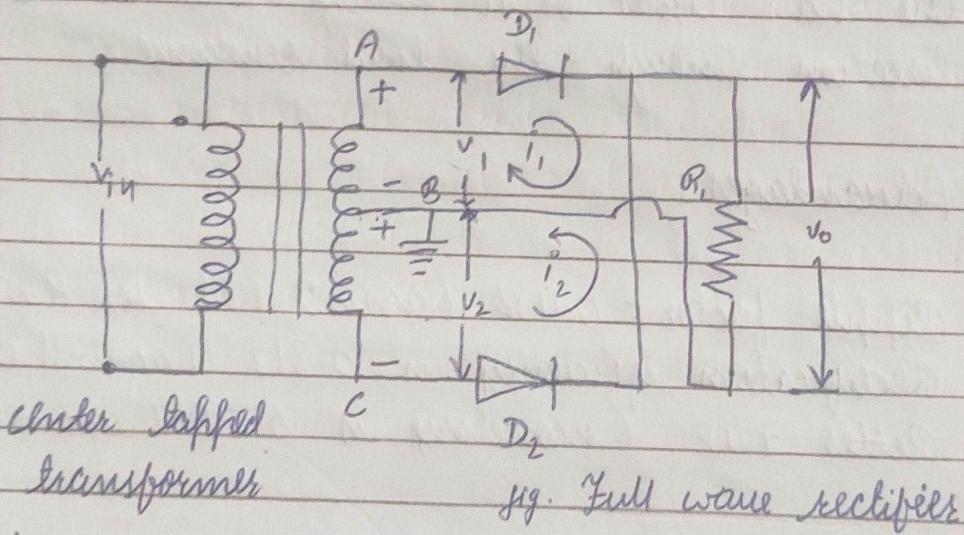


fig. Full wave rectifier

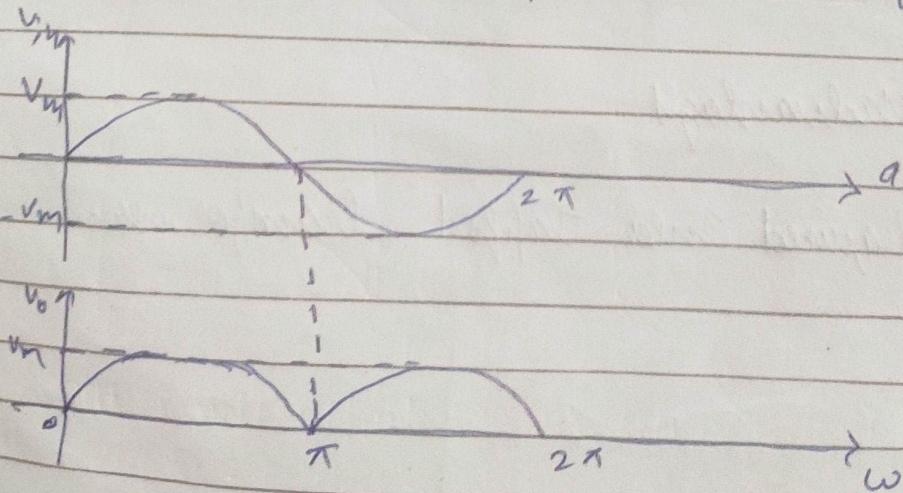

input and output waveforms of fullwave rectifier.

During positive half of the input signal, anode of diode D<sub>1</sub> becomes positive and the anode of diode D<sub>2</sub> becomes negative. Hence D<sub>1</sub> conducts and D<sub>2</sub> does not conduct. The load current flows through D<sub>1</sub> and the voltage drop across R<sub>L</sub> will be equal to the input voltage.

During the negative half cycle of the input the anode of D<sub>1</sub> becomes negative and the anode of D<sub>2</sub> becomes positive. Hence, D<sub>1</sub> does not conduct and D<sub>2</sub> conducts. The load current flows through D<sub>2</sub> and the voltage drop across will be equal to the input voltage. It is noted that the load current flows in the same half cycles of ac voltage and in the same direction through the load resistance.

### Advantages:

- 1) Ripple factor = 0.482 (against 1.21 for HWR)
- 2) Rectification efficiency is 0.812 (against 0.405)
- 3) Better TUF (secondary is 0.574 against 0.287)

### Disadvantages

- 1) Required center tapped transformer.

## Comparison :-

No.	Parameter	MINOR	FWO
1	No. of diodes	1	2
2.	PIV of diode	$V_m$	$2V_m$
3	Secondary voltage (rms)	$V$	$V_D = V$
4.	Ripple factor $\gamma$	1.21	0.482
5.	Rectification efficiency	0.406	0.812

input  
and H  
DI does  
current  
across  
it is  
the h  
name

R)

0.405 to  
0.287 A

## Clamping Circuit :-

The circuit which is not change input signal wave form it will little move up or down. It is also known as 'd.c. inserter' circuit.

Capacitor store the input energy.


Classification of clamping circuit:-

Primarily clamps are of two types.

- (i) Negative clamp (or positive peak clumper)
- (ii) Positive clamp (or negative peak clumper)

If the in-

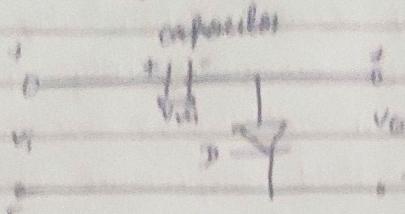(i) Negative clamp (or Positive peak clammer)



If the input voltage is positive then it is enough for the diode to conduct 0.7V.

If the circuit is in on state the energy stored in the capacitor. The maximum voltage across it is  $V_m$ .


KVL equation :-

$$\left. \begin{aligned} V_i - V_m - V_D &= 0 \\ V_D &= V_i - V_m \end{aligned} \right\}$$

if  $V_i = V_m$   
then  $V_D = 0$ .

if  $V_i = 0$   
 $V_D = -V_m$


if  $V_i = -V_m$   
 $V_D = -2V_m$

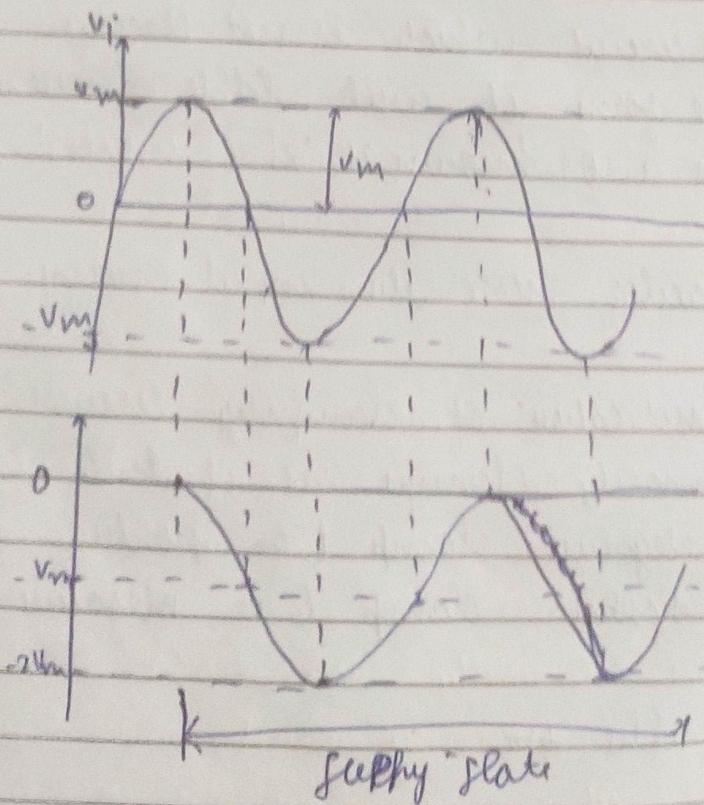


(ii) Positive cl

KVL equation

$$\text{if } V_i = 0 \\ V_o = V_m$$

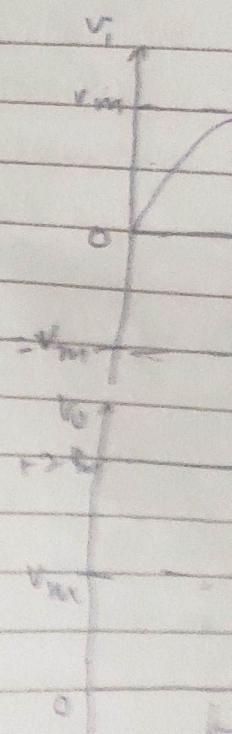

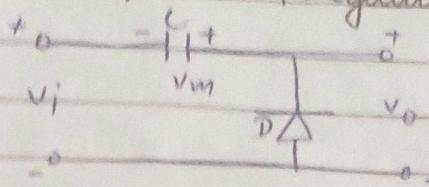(ii) Positive clamp :- (Negative peak clamping)



KVL equation : (clockwise)

$$V_i + V_m - V_o = 0$$

$$V_o = V_i + V_m$$

[E. In C.C. goes from  
-ve to +ve]

$$\text{if } V_i = 0$$

$$V_o = V_m$$


$$\text{if } V_i = V_m$$

$$V_o = 2V_m$$

$$\text{if } V_i = -V_m$$

$$V_o = 0$$

it is on  
energy  
age at u

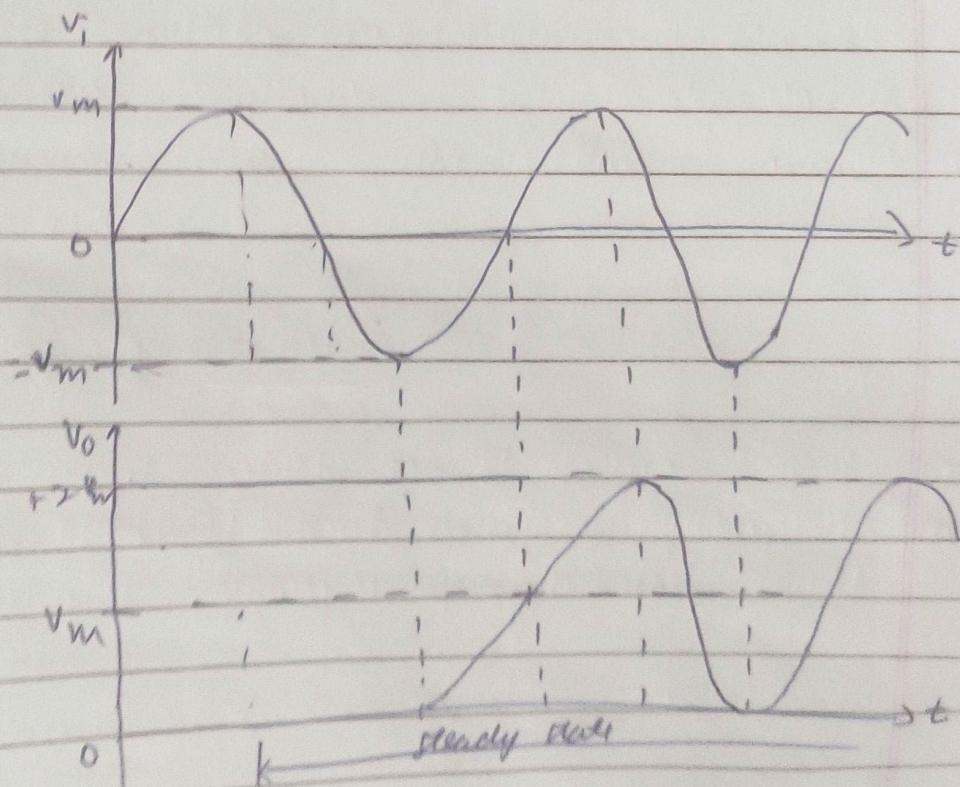

QD